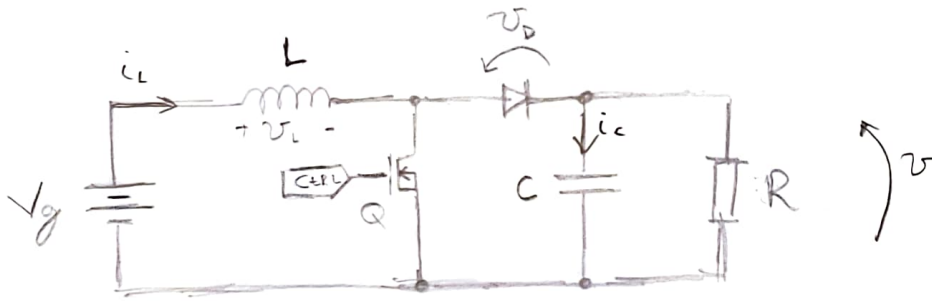


DC BOOST CONVERTER ANALYSIS



1.) Q ON:

- $v_L = V_g$
- $i_c = -\frac{v}{R}$

2.) Q OFF:

- $V_g - v_L - v_D - v = 0$
 $\Rightarrow v_L = V_g - (v + v_D)$
- $i_c = i_L - \frac{v}{R}$

ASSUMING WE DESIRE SMALL RIPPLE:

$\therefore v \approx V = C \Delta v$; $v_D \approx V_D = C \Delta v$

$i_L \approx I = C \Delta i$


\Rightarrow 1.) Q ON:

- $v_L = V_g$
- $i_c \approx -\frac{V}{R}$

2.) Q OFF:

- $v_L \approx V_g - (V + V_D)$
- $i_c \approx I - \frac{V}{R}$

THEN:

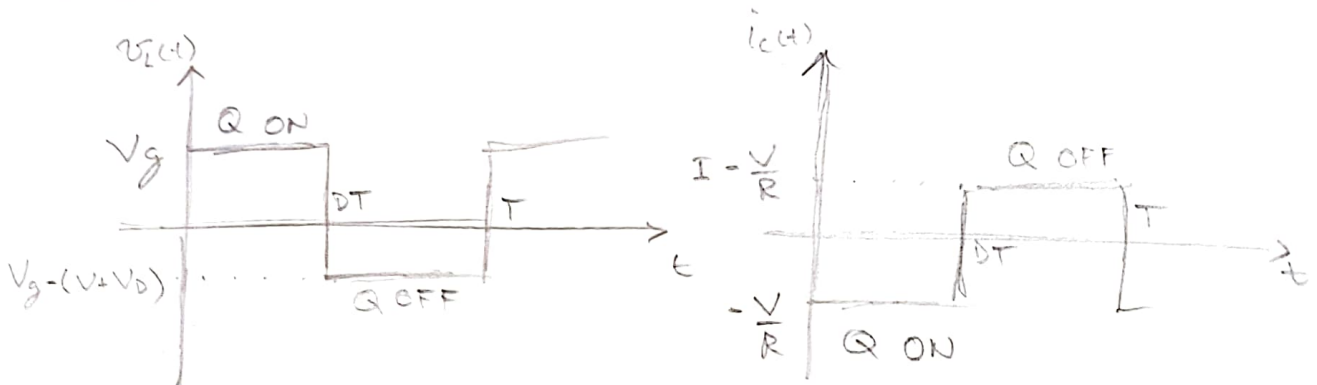

$0 < D < 1$: DUTY CYCLE

CONVERSION RATIO: $M(D)$

$$M(D) = \frac{V}{V_g} \quad (1)$$

ON STEADY-STATE CONDITION (INDUCTOR VOLT-SECOND BALANCE), GIVES US:

$$i_L(T) - i_L(0) = 0 \Rightarrow \frac{1}{L} \int_0^T v_L(t) dt = 0$$

$$\Rightarrow V_g \cdot DT + (V_g - V - V_D) \cdot (1-D) \cdot T = 0$$

$$\Rightarrow V_g \cdot T - V(1-D) \cdot T - V_D(1-D)T = 0$$

$$\Rightarrow \frac{V_g}{(1-D)} = V + V_D \Rightarrow \frac{V}{V_g} = \frac{1}{1-D} - \frac{V_D}{V_g}$$

$$\Rightarrow \boxed{M(D) = -\frac{V_D}{V_g} + \frac{1}{1-D}} \quad (2)$$



WE ALSO KNOW THAT, ON STEADY-STATE:

$$\int_0^T i_L(t) dt = 0 \Rightarrow -\frac{V}{R} \cdot DT + \left(I - \frac{V}{R}\right) (1-D)T = 0$$

$$\Rightarrow -\frac{V}{R} \cdot T + I(1-D)T = 0 \Rightarrow I = \frac{V}{R} \cdot \frac{1}{1-D}$$

$$\Rightarrow \boxed{I = \frac{V_g}{R} \cdot \frac{1}{(1-D)^2} - \frac{V_D}{R} \cdot \frac{1}{(1-D)}} \quad (3)$$

AC ANALYSIS:

1.) Q ON:


$$v_L(t) = V_g \Rightarrow L \frac{di_L}{dt} = V_g \Rightarrow \frac{di_L}{dt} = \frac{V_g}{L}$$

2.) Q OFF:

$$v_L(t) = V_g - (V + V_D) \Rightarrow \frac{di_L}{dt} = \frac{V_g - (V + V_D)}{L}$$

Assuming
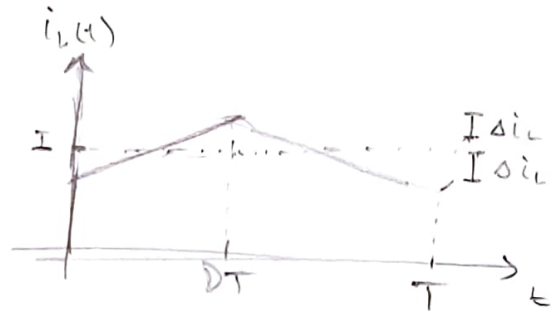
$$i_L \in [I - \Delta i_L, I + \Delta i_L]$$



$$\Rightarrow 2\Delta i_L = \frac{V_g}{L} \cdot DT \Rightarrow \boxed{\Delta i_L = \frac{V_g}{2L} \cdot DT} \quad (4)$$

OR

$$-2\Delta i_L = \frac{V_g - (V + V_D)}{L} (1-D) \cdot T$$

LIKEWISE, FOR THE CAPACITOR WE HAVE:

1.) Q ON:

$$i_C(t) = C \frac{dV}{dt} \Rightarrow \frac{dV}{dt} \approx -\frac{V}{RC}$$


2.) Q OFF:

$$i_C(t) = C \frac{dV}{dt} \Rightarrow \frac{dV}{dt} \approx \frac{I}{C} - \frac{V}{RC}$$

SIMILAR TO THE PREVIOUS ANALYSIS:

$$2\Delta V = -\frac{V}{RC} DT \Rightarrow \boxed{\Delta V \approx \frac{V}{2RC} \cdot DT} \quad (5)$$

INCLUDING INDUCTOR LOSS :

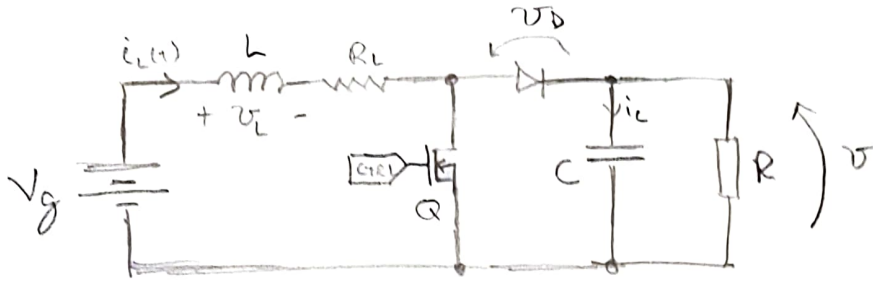

1.) Q ON:

- $v_L = V_g - i_L \cdot R_L$
- $i_C = -\frac{V}{R}$

2.) Q OFF:

- $v_L = V_g - (V + V_D) - i_L \cdot R_L$
- $i_C = i_L - \frac{V}{R}$

ASSUMING SMALL RIPPLE:

1.) Q ON:

- $v_L = V_g - I \cdot R_L$
- $i_C = -\frac{V}{R}$

2.) Q OFF:

- $v_L = V_g - (V + V_D) - I \cdot R_L$
- $i_C = I - \frac{V}{R}$

ON STEADY-STATE:

$$\bullet (V_g - I \cdot R_L) \cdot DT + [V_g - (V + V_D) - I \cdot R_L] (1-D)T = 0$$

$$\Rightarrow \boxed{0 = V_g - I R_L - (1-D)(V + V_D)} \quad (6)$$

$$\bullet -\frac{V}{R} \cdot DT + \left(I - \frac{V}{R}\right) (1-D)T = 0 \Rightarrow \boxed{I = \frac{V}{R} \cdot \frac{1}{1-D}} \quad (7)$$

FROM (7) IN (6):

$$V_g = V \cdot \frac{R_L}{R} \cdot \frac{1}{1-D} + (1-D)V + (1-D)V_D$$

$$V_g - (1-D)V_D = V \left[\frac{R_L}{R} \cdot \frac{1}{1-D} + (1-D) \right]$$

$$\Rightarrow \left[\frac{V}{V_g} = -\frac{V_D}{V_g} \cdot \frac{1}{1 + \frac{R_L}{R} \cdot \frac{1}{(1-D)^2}} + \frac{1}{(1-D)} \cdot \frac{1}{1 + \frac{R_L}{R} \cdot \frac{1}{(1-D)^2}} \right] \quad (8)$$

EFFICIENCY:

$$\eta = \frac{P_{out}}{P_{in}} ;$$

$$\left. \begin{array}{l} \bullet P_{in} = V_g \cdot I \\ \bullet P_{out} = V \cdot \frac{V}{R} \end{array} \right\} \Rightarrow \eta = \frac{V}{V_g} \cdot \frac{1}{RI} \stackrel{(4)}{=} \frac{V}{V_g} \cdot (1-D)$$

$$\Rightarrow \left[\eta = -\frac{V_D}{V_g} \cdot \frac{(1-D)}{1 + \frac{R_L}{R} \cdot \frac{1}{(1-D)^2}} + \frac{1}{1 + \frac{R_L}{R} \cdot \frac{1}{(1-D)^2}} \right] \quad (9)$$

INCLUDING SEMICONDUCTOR LOSSES:

$$\left[\frac{V}{V_g} = -\frac{V_D}{V_g} \cdot \frac{1}{1 + \frac{R_L + D \cdot R_{on} + (1-D)R_D}{R(1-D)^2}} + \frac{1}{(1-D)} \cdot \frac{1}{1 + \frac{R_L + D \cdot R_{on} + (1-D)R_D}{R(1-D)^2}} \right] \quad (10)$$

$$\text{LET } \left[\gamma(D) = \frac{1}{1 + \frac{R_L + D \cdot R_{on} + (1-D)R_D}{R(1-D)^2}} \right] \quad \text{THE LOSS FACTOR} \quad (11)$$


THEN:

$$M(D) = \gamma(D) \cdot \left[-\frac{V_D}{V_g} + \frac{1}{1-D} \right] \quad (12)$$

$$\eta = \gamma(D) \left[1 - (1-D) \cdot \frac{V_D}{V_g} \right] \quad (13)$$

DISCONTINUOUS MODE ANALYSIS:

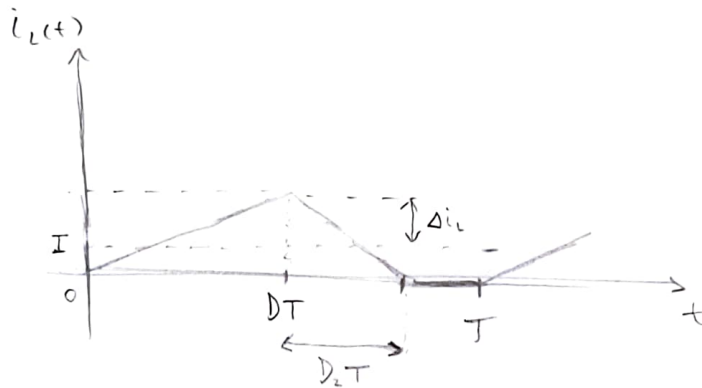DISCONTINUOUS CONDUCTION MODE (DCM) HAPPENS WHEN $i_L(t)$ GOES TO ZERO, THEN NO CURRENT FLOWS THROUGH THE DIODE



THEN, THE CONDITION TO STAY IN CONTINUOUS CONDUCTION MODE (CCM) IS:

$$I > \Delta i_L \quad (14)$$

ASSUMING ALL LOSSES:

Q ON: $v_L(t) \approx V_g - R_L \cdot I = L \cdot \frac{di_L}{dt} \Rightarrow \frac{di_L}{dt} \approx \frac{(V_g - R_L \cdot I)}{L}$

THEN:

$$\Delta i_L = \frac{V_g \cdot DT}{2L} - \frac{R_L I \cdot DT}{2L} \quad (15)$$

FROM (15) IN (14):

$$I > \frac{V_g \cdot DT}{2L} - \frac{R_L I \cdot DT}{2L}$$

$$\Rightarrow I \left[1 + \frac{R_L DT}{2L} \right] > \frac{V_g \cdot DT}{2L}$$

$$\xrightarrow{(1), (7)} \frac{V_g}{R} \cdot \frac{M(D)}{1-D} \left[1 + \frac{R_L DT}{2L} \right] > \frac{V_g \cdot DT}{2L}$$

$$\Rightarrow \boxed{\frac{2L}{RT} > \frac{D(1-D)}{M(D)} \left[1 - \frac{R_L}{R} \cdot \frac{M(D)}{1-D} \right]} \quad (16)$$

LET

$$\left\{ K = \frac{2L}{RT} \quad (17) \right.$$

$$\left. K_{crit}(D) = \frac{D(1-D)}{M(D)} \left[1 - \frac{R_L}{R} \cdot \frac{M(D)}{1-D} \right] \quad (18) \right.$$

ASSUMING NO LOSSES:

$$K_{crit}(D) = \frac{D(1-D)}{M(D)}$$

ASSUMING IDEAL DIODE, FROM (2):

$$M(D) = \frac{1}{1-D} \quad \therefore K_{crit}(D) = D(1-D)^2$$

$$\Rightarrow \max_{0 < D < 1} \{K_{crit}(D)\} = \frac{4}{27}$$

THEN

$$\boxed{\frac{2L}{RT} > \frac{4}{27}} \quad \text{GUARANTEE CCM WHEN NO LOSSES} \quad (19)$$

ARE CONSIDERED AND ASSUMING IDEAL DIODE.

